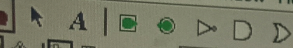


4-bit-Carry-Look-ahead-Adder-Logic-Diagram

A	B	C_i	C_{i+1}	Condition
0	0	0	0	No carry generate
0	0	1	0	
0	1	0	0	
0	1	1	1	No carry propagate
1	0	0	0	
1	0	1	1	
1	1	0	1	Carry generate
1	1	1	1	

Carry-Look-ahead-Adder-Truth-Table



- Untitled 2*
- main
 - Wiring
 - Gates
 - NOT Gate
 - Buffer
 - AND Gate
 - OR Gate
 - NAND Gate
 - NOR Gate
 - XOR Gate
 - XNOR Gate
 - Odd Parity
 - Even Parity
 - Controlled B...
 - Controlled In
 - Plexers
 - Arithmetic

Pin	
acing	East
output?	No
ata Bits	1
three-state?	No
ull Behavior	Unchanged
label	
label Location	West
label Font	SansSerif P...

